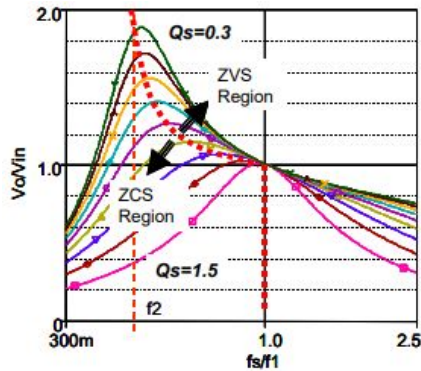


# LLC Resonant Converter: Operation and Application


By: Noah Bean and Cade Tillema

# Circuit Functionality

- Makes use of inherent transformer properties
- Resonance




Soft-switching regions [1]

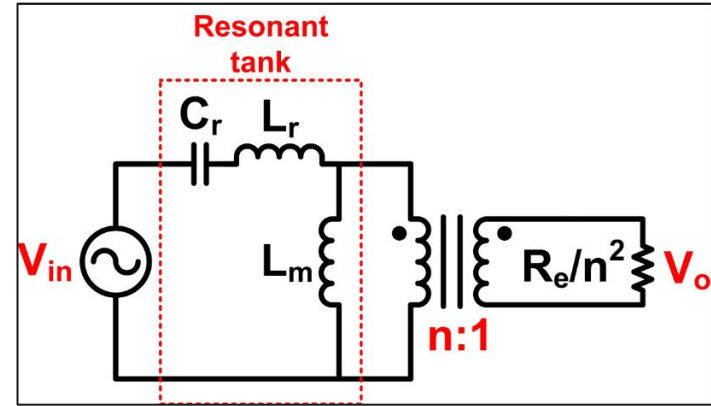

$$f_R = \frac{1}{2\pi\sqrt{L_R \times C_R}}$$


$$f_M = \frac{1}{2\pi\sqrt{L_M + L_R \times C_R}}$$

# Circuit Functionality

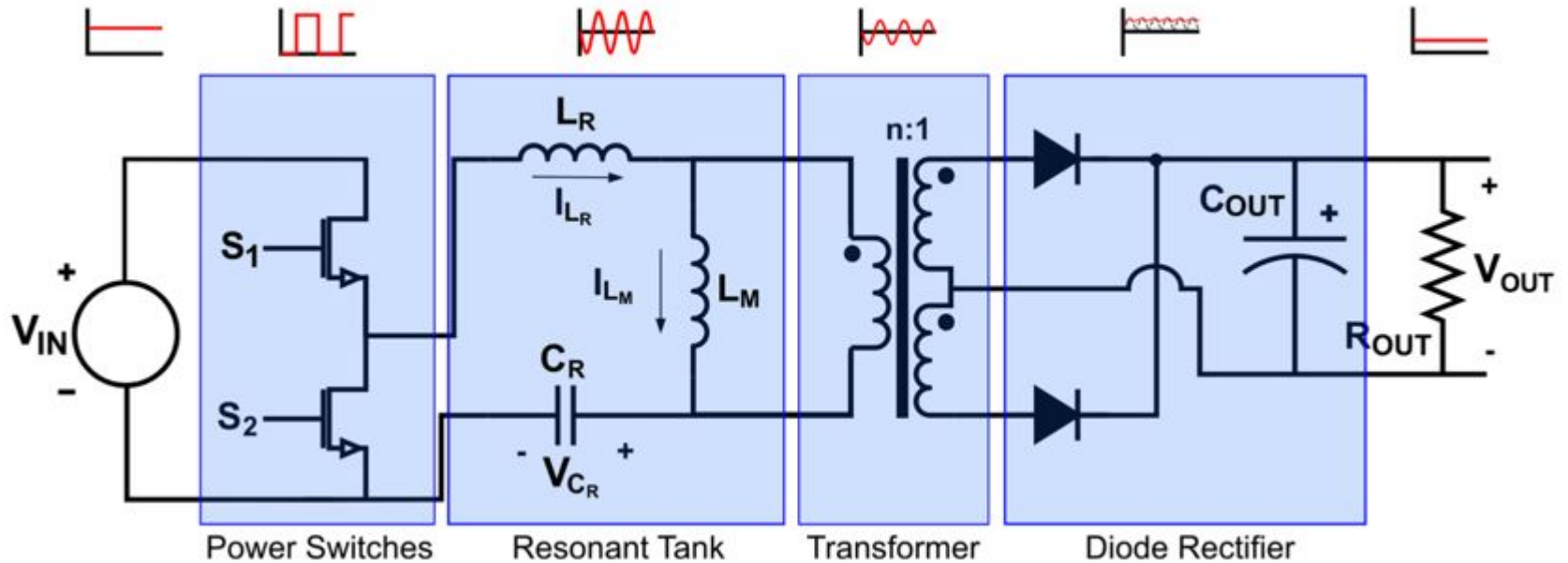


# LLC Modes of Operation [1]

Mode 1

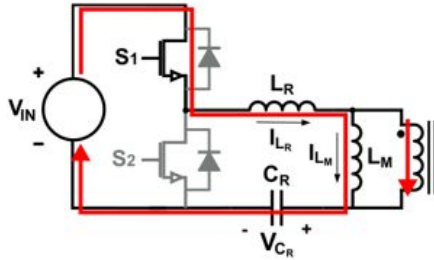


Mode 2

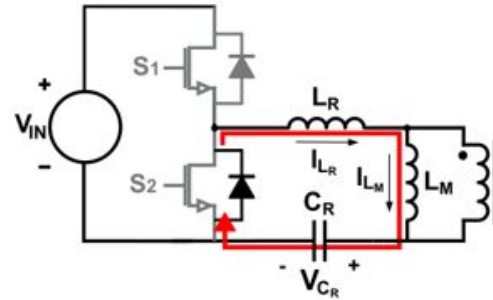


“Dead Period”


Mode 3

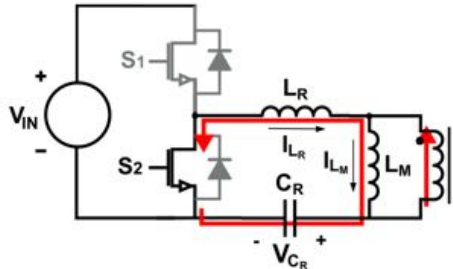




Mode 4

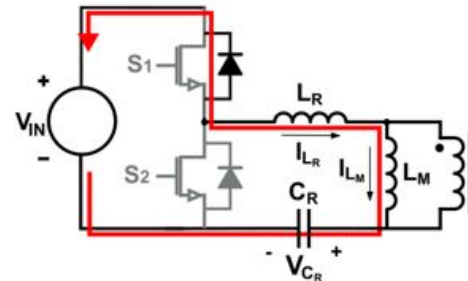




“Dead Period”

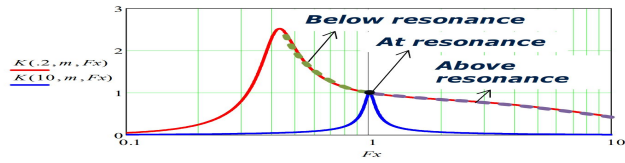

## Power Delivery ( $f_s = f_r$ )

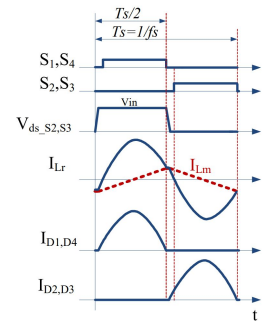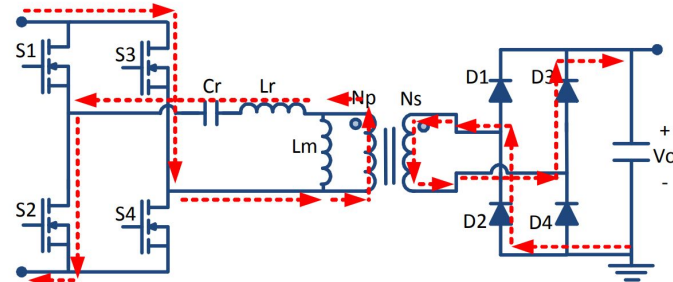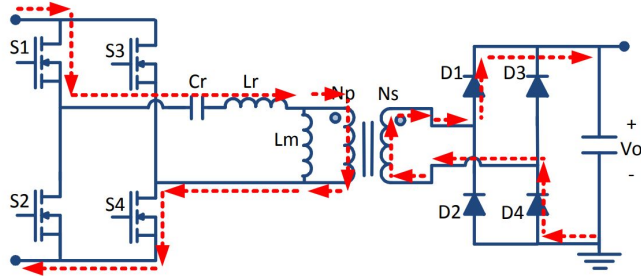

## Free Wheeling ( $f_s > f_r$ )

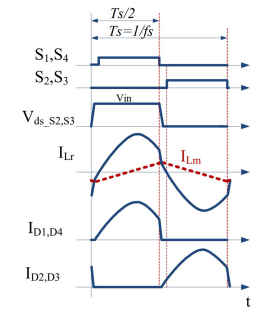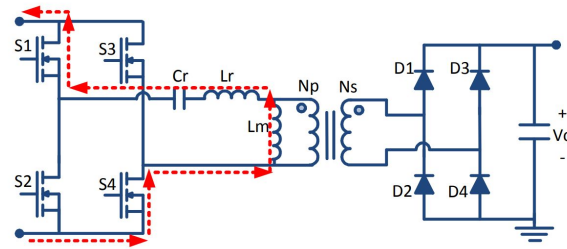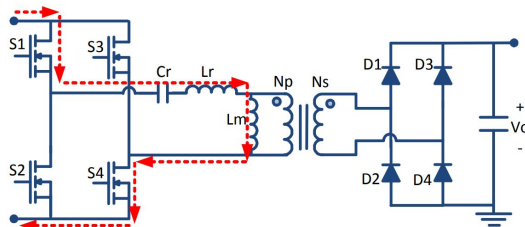

# Design Considerations

- Choose Half-Bridge or Full Bridge
- Choose Mode of Operation  
 $f_s = f_r \rightarrow$  full power  
 $f_s > f_r \rightarrow$  partial power (buck)  
 $f_s < f_r$  (boost)
- Choose values for the  $L_m$ ,  $L_r$ , and  $C_r$
- Chose a control strategy for inverter
- Manage heat dissipation in diodes and MOSFETs

$$K(Q, m, F_x) = \frac{|V_{o\_ac}(s)|}{|V_{in\_ac}(s)|} = \frac{F_x^2 (m-1)}{\sqrt{(m \cdot F_x^2 - 1)^2 + F_x^2 \cdot (F_x^2 - 1)^2 \cdot (m-1)^2 \cdot Q^2}}$$

$$Q = \frac{\sqrt{L_r / C_r}}{R_{ac}}$$

Quality factor

$$R_{ac} = \frac{8}{\pi^2} \cdot \frac{N_p^2}{N_s^2} \cdot R_o$$

Reflected load resistance

$$F_x = \frac{f_s}{f_r}$$


Normalized switching frequency

$$f_r = \frac{1}{2\pi \sqrt{L_r \cdot C_r}}$$

Resonant frequency

$$m = \frac{L_r + L_m}{L_r}$$

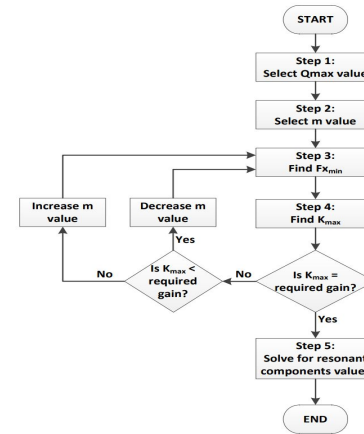
Ratio of total primary inductance to resonant inductance



# Advantages and Disadvantages

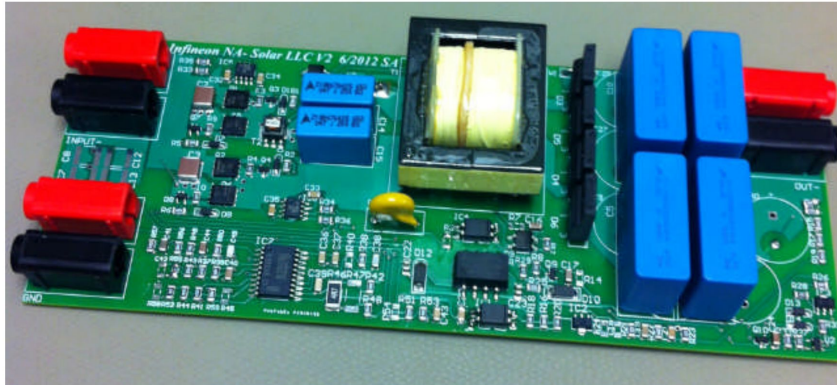
## Advantages

- High efficiency (soft switching: ZVS, ZCS)
- Reduced component size (high frequency)
- Wide input voltage range (robust input)
- Reduced electromagnetic interference (EMI)
- Isolated input and output (transformer)


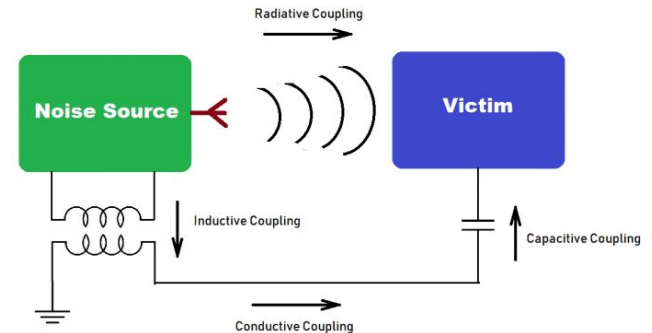
## Disadvantages

- Load sensitivity (non-linear)
- Control complexity (inverters)
- System and component cost



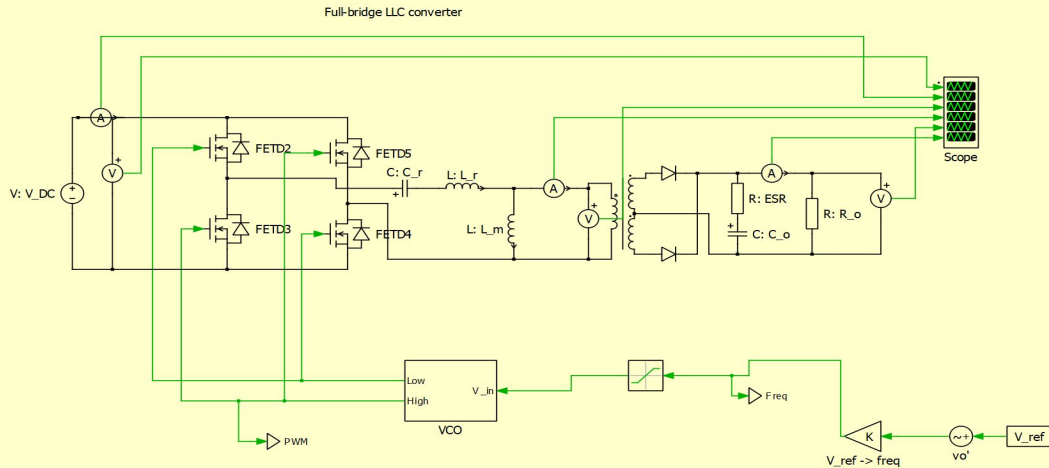
# Applications

- LED lighting (efficiency)
- Photovoltaic inverters (efficiency)
- Electric vehicle chargers (compact system size)
- Telecommunications (low EMI)
- Data center servers (low EMI)








This project aims to design and simulate an LLC resonant converter for an electric car battery

Design Requirements  
input voltage  $v_{dc} = 80 \text{ v}$   
output voltage  $v_0 = 22.8 \text{ v}$   
switching frequency  $f_s = 100 \text{ kHz}$   
rated power  $p_r = 5.3 \text{ kw}$   
Efficiency  $\eta > .9$   
 $I_{out} = 190 \text{ A}$

Component Specifications



- $I_m = 1.4e-4$  H
- $I_r = 2.79e-5$  H
- $\sigma = 9.09e-9$  F
- $Q = 0.5$
- $m = 6$
- $Q_{max} = 0.4$
- $R_{aC\_min} = 35$  ohms
- $N = 10:1$

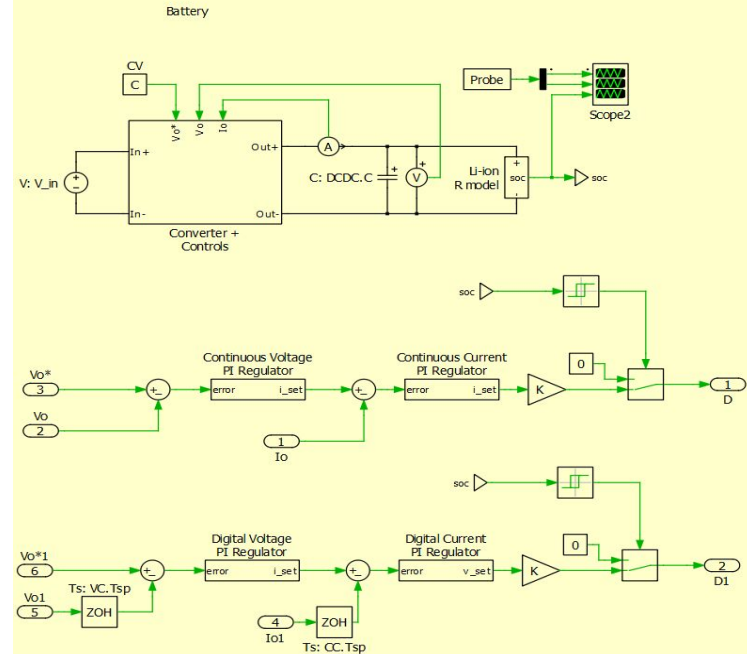
Battery Specifications for Tesla Model S Lithium Ion Battery  
Capacity: 232Ah, 5.3kWh,  
Voltage nominal: 3.8V/Cell, 22.8V/Module  
Charge voltage cut-off: 4.2V/Cell, 25.2V/Module  
Discharging cut-off: 3.3V/Cell, 19.8V/Module  
Maximum Discharging Current (10 sec.): 750 Amps




# Simulation Results (LLC Converter)

THD of input current THD meets IEEE 519				
Bus voltage V at PCC	Individual harmonic (%)	THD (%)	Individual harmonic (%)	THD (%)
V ≤ 1.0 kV	5.0	8.0	7.5	12

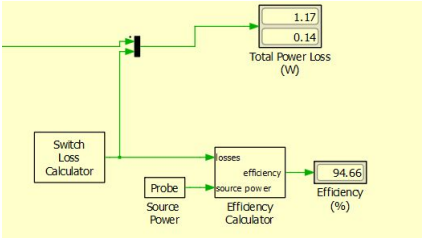
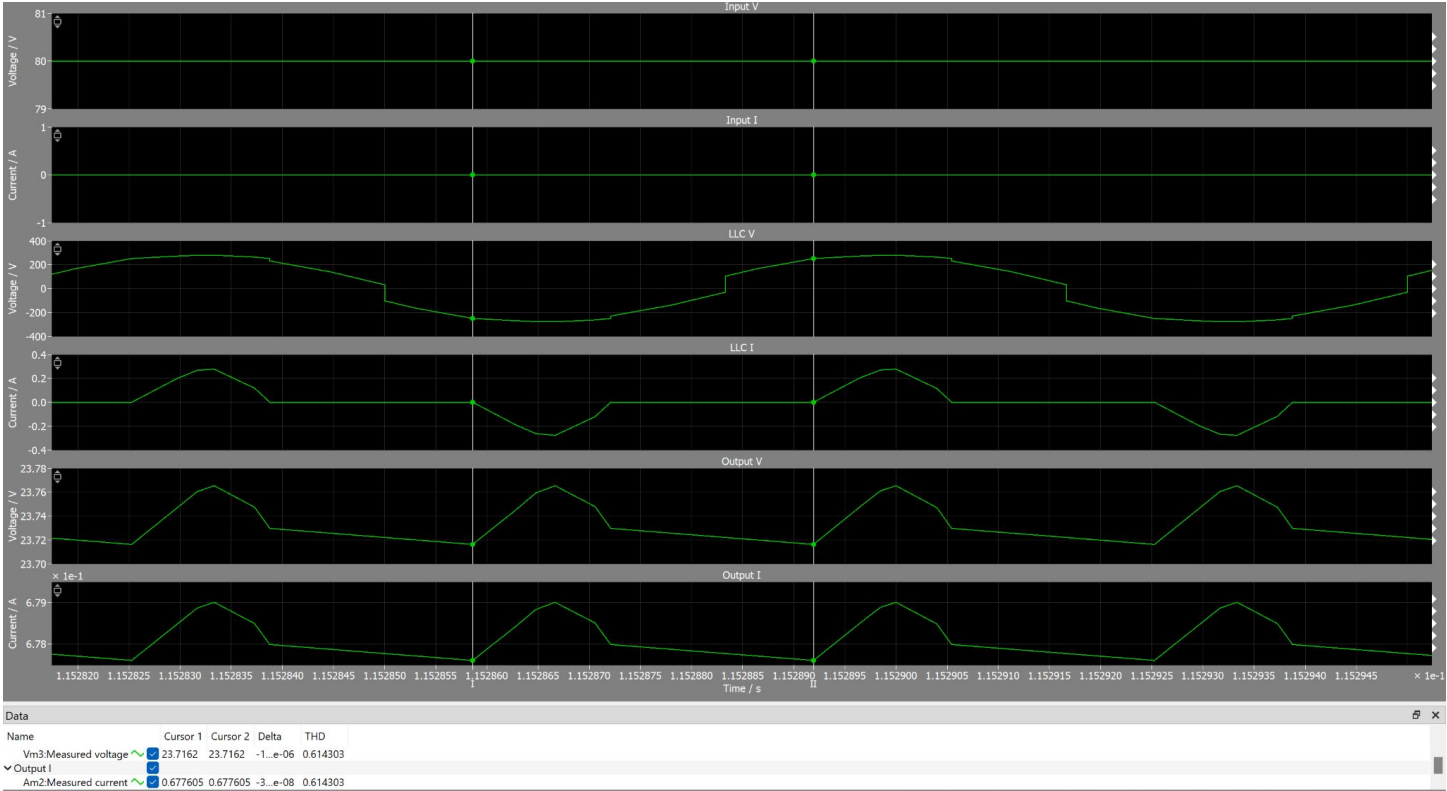


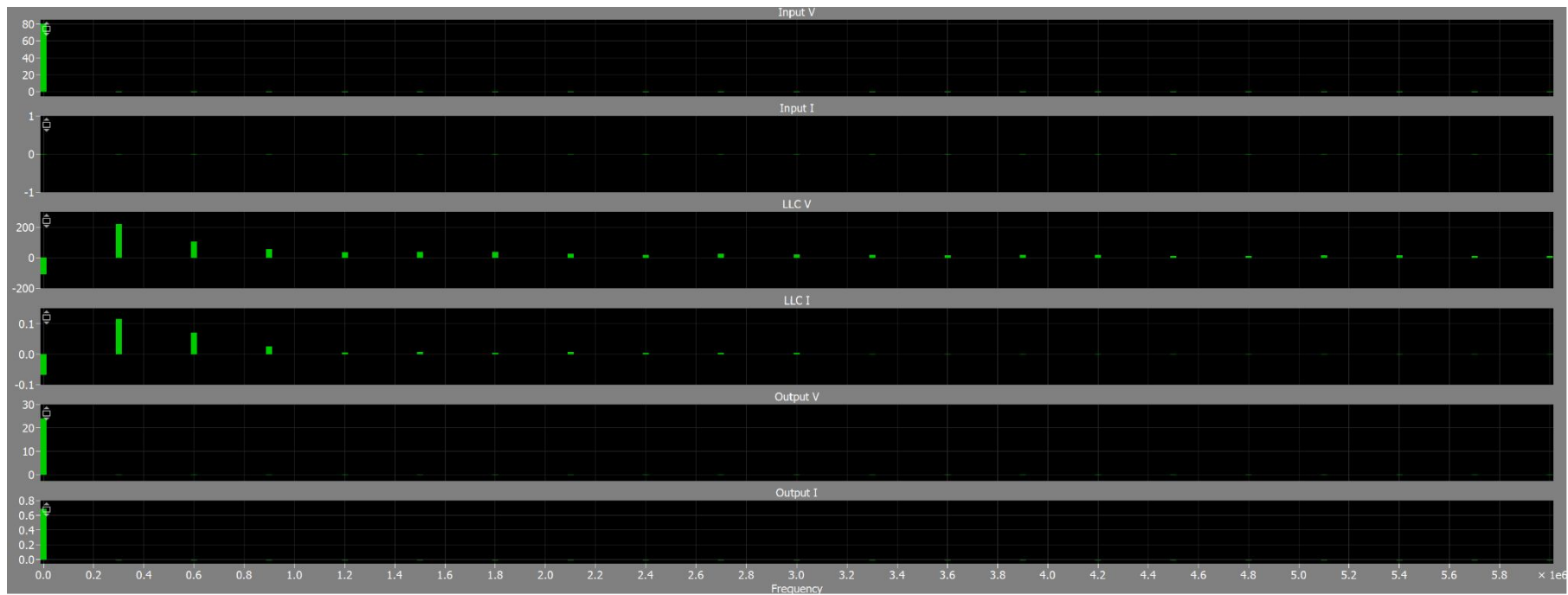
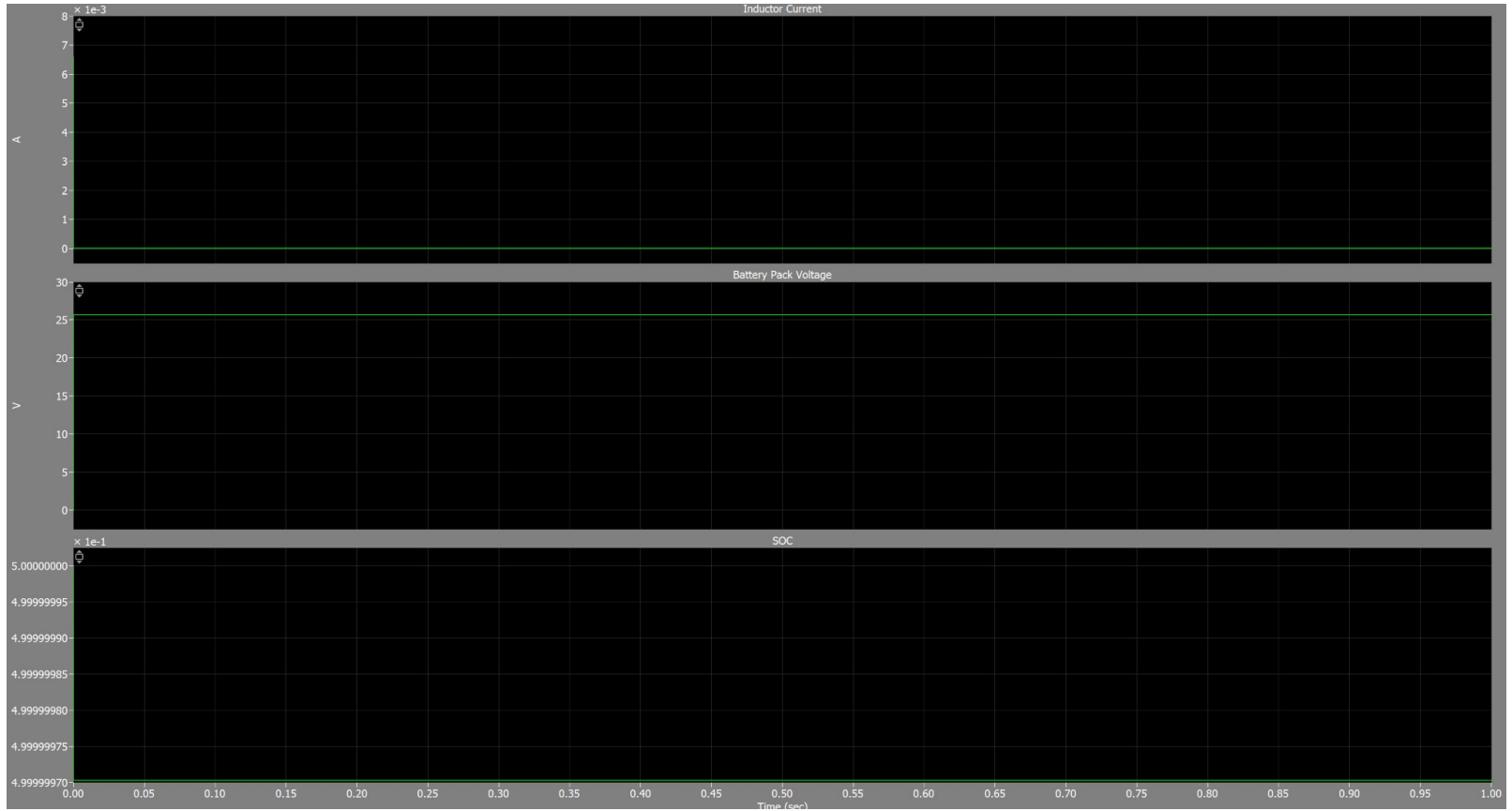
# Simulation Results (Electric Car Battery)



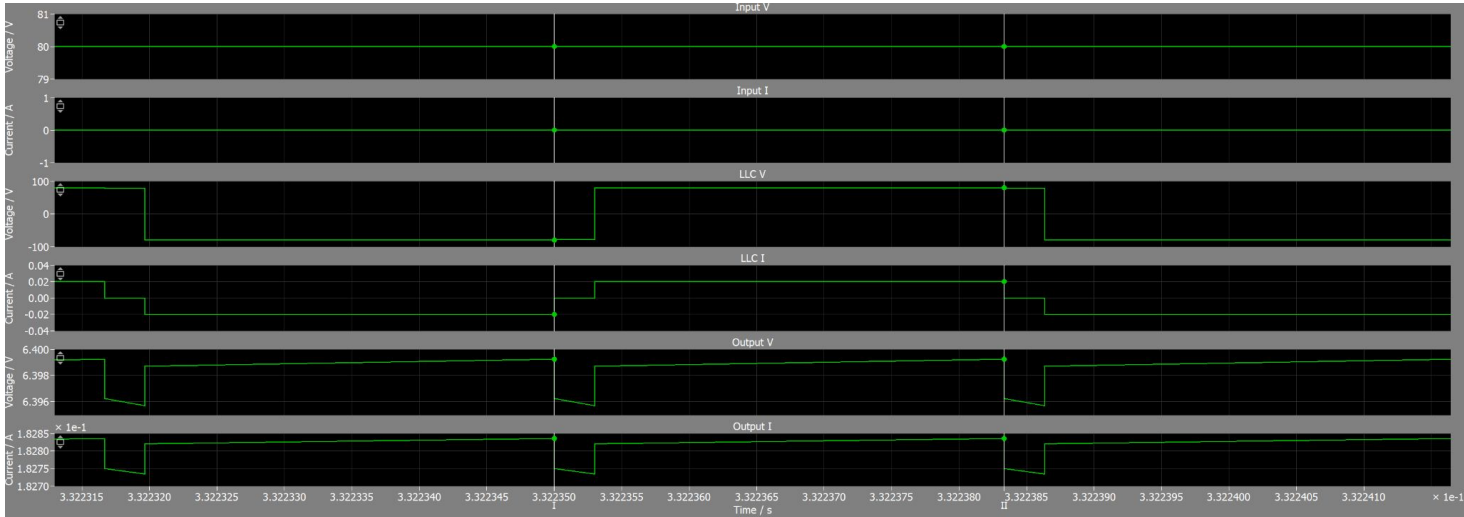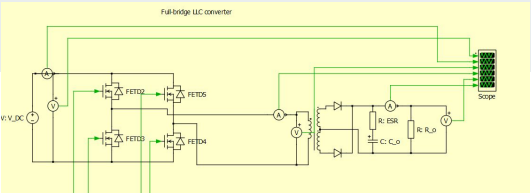
# Simulation Results (Without resonant tank)




Data					
Name	Cursor 1	Cursor 2	Delta	THD	
Time	0.332235	0.332238	...e-06		
Input V	<input checked="" type="checkbox"/>				
VCO Input Voltage	<input checked="" type="checkbox"/> 80	80	0	0	
Input I	<input checked="" type="checkbox"/>				
Output Current	<input checked="" type="checkbox"/> 0	0	0	0	
LLC V	<input checked="" type="checkbox"/>				
Vm4:Measured voltage	<input checked="" type="checkbox"/> -79.9988	79.9988	-159.998	2.04755	
LLC I	<input checked="" type="checkbox"/>				
Am1:Measured current	<input checked="" type="checkbox"/> -0.0200...	0.02006...	-0.0401...	2.04757	
Output V	<input checked="" type="checkbox"/>				
Vm3:Measured voltage	<input checked="" type="checkbox"/> 6.39925	6.39925	-8...e-15	1.94208	
Output I	<input checked="" type="checkbox"/>				
Am2:Measured current	<input checked="" type="checkbox"/> 0.182836	0.182836	-2...e-16	1.94208	


# LED Driver Application - Cade

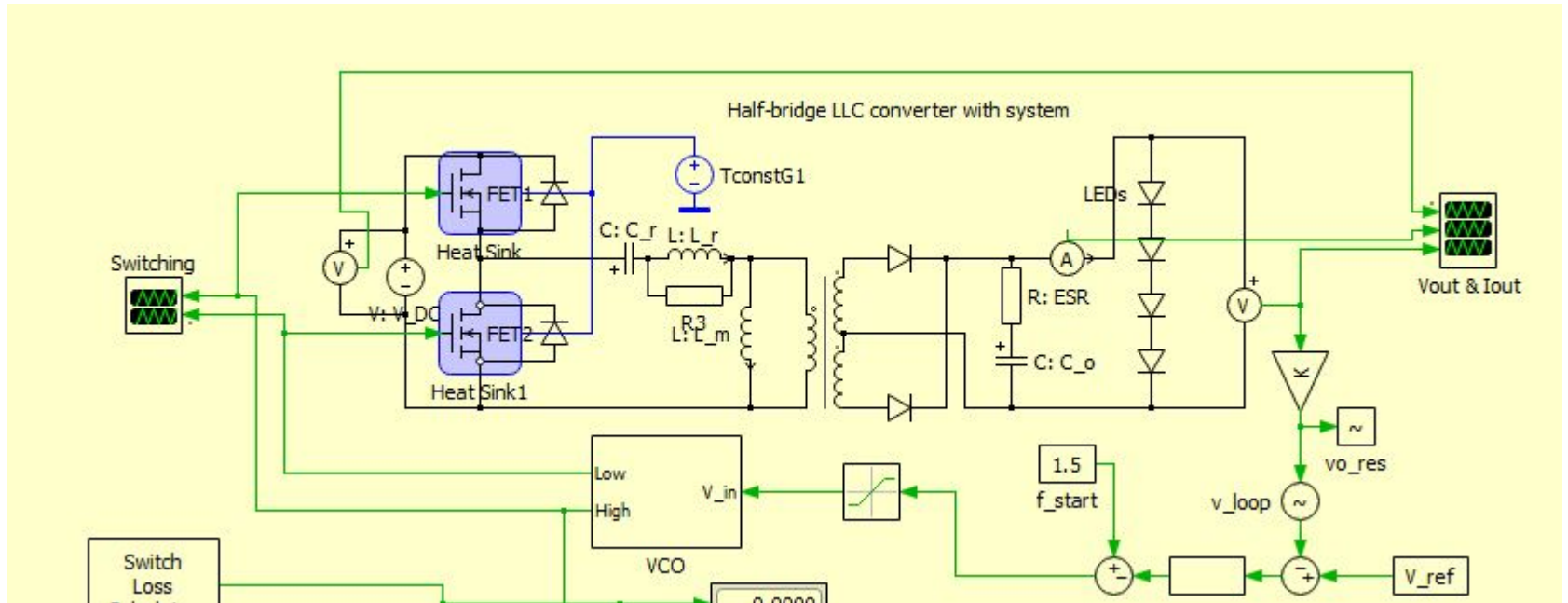


# Output Voltage

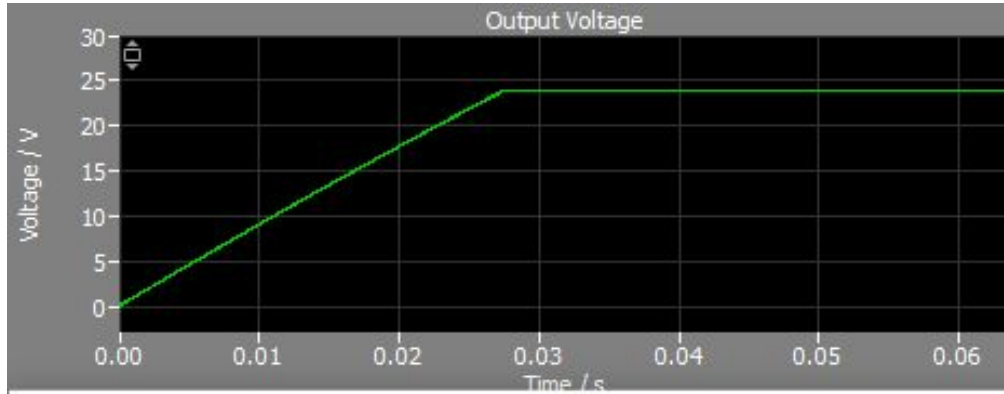

Voltage across single Diode

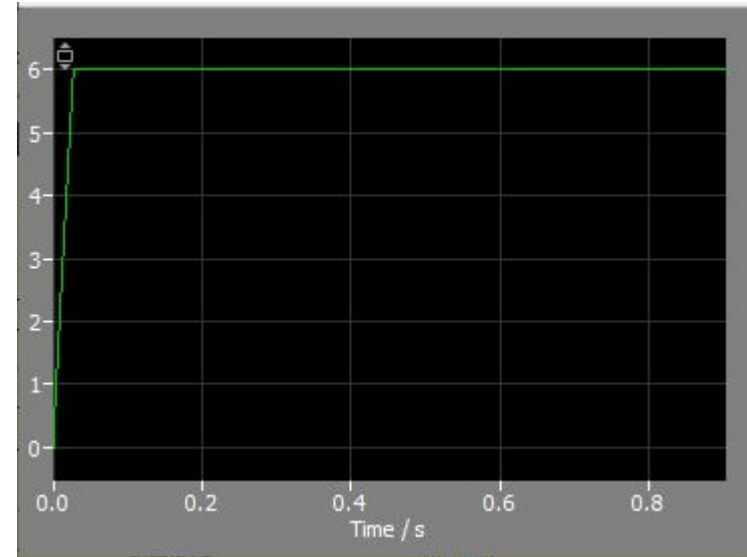

# LED Driver Application - Cade

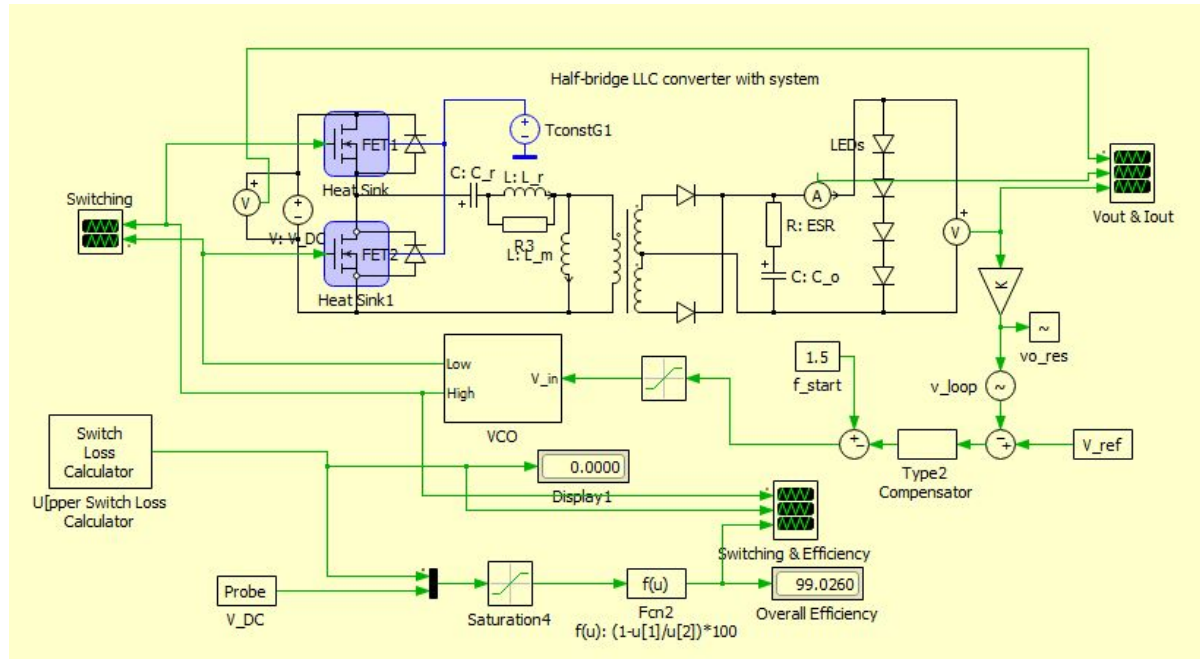



# Switching Waveform



# Conclusion



Noah:

Objective evaluation:

- Design for LLC Resonant converter was successful (THD, output voltage, efficiency)
- Battery Model was successful (SOC, output voltage)
- Integration with battery model and converter was unsuccessful (required changing Matlab Code)

Lessons:


- Learn how to use Matlab for system integration with PLECS initialization
- Learned more about designing circuits and using PLECS

Future Efforts:

- Investigate control systems
- Investigate magnetic circuit considerations
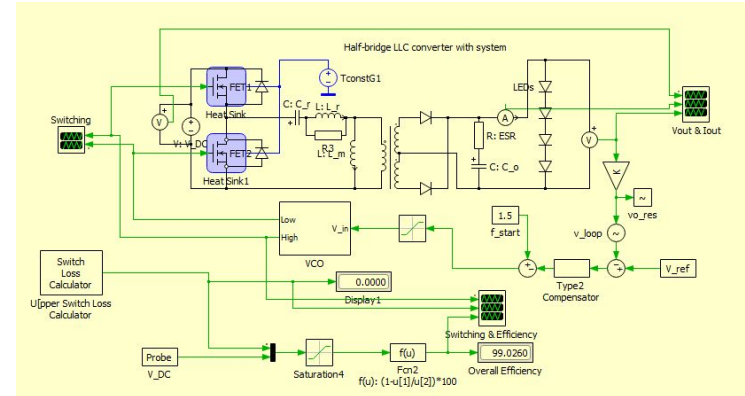
# Conclusion - Cade

- Achieved very high efficiency
- Needed more realistic load
- Learned how to use many different resources





## References

- [1] Bo Yang, F. C. Lee, A. J. Zhang and Guisong Huang, "LLC resonant converter for front end DC/DC conversion," APEC. Seventeenth Annual IEEE Applied Power Electronics Conference and Exposition (Cat. No.02CH37335), Dallas, TX, USA, 2002, pp. 1108-1112 vol.2, doi: 10.1109/APEC.2002.989382
- [2]"Understanding LLC Operation (Part I): Power Switches and Resonant Tank | Article | MPS," *Monolithicpower.com*, 2022. <https://www.monolithicpower.com/understanding-llc-operation-part-i-power-switches-and-resonant-tank>



## References

[3] S. Abdel-Rahman, "Resonant LLC Converter: Operation and Design 250W 33Vin 400Vout Design Example," 2012. Available:

[https://www.infineon.com/dgdl/Application\\_Note\\_Resonant+LLC+Converter+Operation+and+Design\\_Infineon.pdf?fileId=db3a30433a047ba0013a4a60e3be64a1](https://www.infineon.com/dgdl/Application_Note_Resonant+LLC+Converter+Operation+and+Design_Infineon.pdf?fileId=db3a30433a047ba0013a4a60e3be64a1)

[4] J. Deng, S. Li, S. Hu, C. C. Mi and R. Ma, "Design methodology of LLC resonant converters for electric vehicle battery chargers", IEEE Trans. Veh. Technol., vol. 63, no. 4, pp. 1581-1592, May 2014

[5] Y. Wei, Q. Luo, Z. Wang and H. A. Mantooth, "A complete step-by-step optimal design for LLC resonant converter", IEEE Trans. Power Electron., vol. 36, no. 4, pp. 3674-3691, Apr. 2021.